

- Asynchronous sequential circuits (*cont.*)
 design of, 415–416
 flow table, 420–422
 fundamental mode, 417
 hazards, 452–457
 in combinational circuits, 452–454
 defined, 452
 detection of, 453
 essential, 456–457
 implementation with SR
 latches, 454–456
 remedy for eliminating, 454
 in sequential circuits, 454
 implementation example, 430–431
 laboratory experiment, 553
 latch excitation table, 430
 logic diagram, 436–437
 primitive flow table, 433–435
 reduction of, 435–436
 race conditions, 422–424
 race-free state assignment, 446–452
 four-row flow-table example, 449–450
 multiple-row method, 450–452
 three-row flow-table example,
 447–449
 reduction of state and flow tables,
 439–446
 closed-covering condition, 445–446
 compatible pairs, 443–444
 implication table and implied states,
 440–442
 maximal compatibles, 444–445
 merging of the flow table, 442–443
SR latch, 425–427, 430–431
 analysis example, 428–429
 transition table, 430
 stability, 424–425
 transition table, 417–420, 436–437
 unstable states:
 assigning outputs to, 437–439
 Asynchronous sequential logic, 415–470
- B**
- Base, 3–4
 BCD 841, 21–22
 BCD adder, 140–142
 block diagram, 141
 BCD addition, 19–20
 BCD (binary-coded decimal) code, 18–19
 BCD ripple counters, 256–258
 logic diagram, 257
 state diagram, 256
 Behavioral modeling, 168–170, 207–210
 Bidirectional shift register, 251, 537,
 537–538
 with parallel load, 537–538
- Binary adder, 133–134
 Binary adder-subtractor, 129–139
 binary adder, 133–134
 binary subtractor, 136–138
 carry propagation, 134–136
 full adder, 131–133
 half adder, 130–131
 overflow, 138–139
- Binary and decimal numbers (laboratory experiment), 516
 BCD count, 517–518
 binary count, 516–517
 counts, 518
 oscilloscope display, 517
 output pattern, 517–518
- Binary cell, 25
- Binary codes, 1, 17–25
 American Standard Code for
 Information Interchange
 (ASCII), 23–25
 BCD 841, 21–22
 BCD addition, 19–20
 BCD (binary-coded decimal)
 code, 18–19
 decimal arithmetic, 20–21
 error-detecting code, 25
 Excess-3 code, 21–22
 Gray code, 22–23
 n-bit binary code, 17–18
 2421 code, 21–22
 weighted codes, 21
- Binary countdown counters, 255
- Binary counter with parallel load, 262–265
 Clear input, 262–264
 CLK input, 264
 Count input, 264
 Load input, 264
- Binary counters:
 defined, 253
 with parallel load, 534–535
- Binary decision box, algorithmic state machines (ASMs), 350
- Binary digits, 1
- Binary logic, 28–31
 defined, 29
 logic gates, 30–31
- Binary multiplier, 142–143
 control state diagram for, 376
 HDL description of, 382–389
 datapath unit, 382
 next-state logic of the controller, 382
- laboratory experiment, 549–553
 block diagram, 549–550
 checking, 552–553
 control of registers, 550–552
 datapath design, 552
- design of control circuit, 552
 multiplication example, 552
 parallel multiplier, behavioral
 description of, 388–390
 testing, 384–388
- Binary numbers, 3–5
 conversion to octal numbers, 9
 signed, 14–17
 sum of, 5
 unsigned, 14
- Binary operator, 36
- Binary ripple counters, 253–256
 binary count sequence, 255
 defined, 253
 four-bit, 254
- Binary storage and registers, 25–28
- Binary storage cell, 291–292
- Binary subtractor, 136–138
- Binary systems, 3–4
- Bipolar IC transistors, 477
- Bipolar junction transistor (BJT), 473
- Bipolar transistors:
 base-emitter graphical
 characteristic, 479
 characteristics of, 477–481
 collector and base currents, 478
 dc current gain, 479
 graphical collector-emitter
 characteristics, 479
 pulled down output, 479
 pulled out output, 479
 saturation region, 479
- Bits, 1, 4, 285
- Bitwise operators, 338
- Block statement, 112
- Blocking assignments, 209–210, 337
- Boole, George, 38
- Boolean algebra, 28, 38
 associative law, 37
 axiomatic definition of, 38–39
 basic theorems, 41–43
 binary operator, 36
 canonical forms, 48–55
 conversion between, 52–53
 closure, 37
 commutative law, 37
 defined, 36, 44
 distributive law, 37
 duality, 41
 field, 37–38
 identity element, 37
 inverse, 37
 and logic gates, 30–31, 36–39
 manipulation of, 46–47
 maxterms, 48–50
 product of, 52

- Control unit, 345–346
 Controllers, 335
 Count operation registers, 334
 Counters:
 binary countdown counters, 255
 defined, 242, 253
 divide-by- N counter, 265
 HDL for, 269–276
 Johnson, 268–269
 laboratory experiment, 533–535
 binary counter with parallel load, 534–535
 decimal counter, 534
 ripple counter, 534
 synchronous counter, 534
 ring, 267–268
 ripple, 253–258
 BCD, 256–258
 binary, 253–256
 symbols, 572–574
 synchronous, 258–264
 with unused states, 265–266
 Critical race, 422–423
 avoiding, 447
 examples of, 423
 Crosspoint, 300
 Cycle time, memory, 289
 Cycles, 423–424
 Cyclic behavior, 207, 343
 edge-sensitive, 344
- D**
- D flip-flops:
 advantage of designing with, 228
 analysis of clocked sequential circuits with, 204–206
 analysis with, 200–201
 characteristic equation, 194
 characteristic table, 193–194
 as example of a sequential machine, 210–212
 D latch (transparent latch), 187–188
 Darlington pair, 490–491
 Data selector, 154
 Dataflow modeling, 165–167
DataIn, 288
DataOut, 288
 Datapath unit, 345–346
 Data-processing path, 345–346
 DC current gain, 479
 Debounce circuit, 431
 Decade counter, 256
 Decimal adder, 139–142
 BCD adder, 140–142
 Decimal arithmetic, 20–21
- Decimal counter, 534
 Declaration, 110
 Decoders, 146–149, 566
 combinational logic
 implementation, 149
 n-to-m-line decoders, 146
 three-to-eight-line, 146
 truth table for, 147
 two-to-four-line, with enable input, 147–148
 Delay control operator, 208
 DeMorgan's theorem, 43, 47–48
 Demultiplexer:
 defined, 148
 with enable input, 147–148
 Dependency notation, 564–566
 Design:
 asynchronous sequential circuits, 433–439, 457–463
 logic diagram, 461–463
 merging of the flow table, 459–460
 primitive flow table, 457–458
 specifications, 457
 state assignment, 460–461
 transition table, 460–461
 combinational circuits, 523
 with complex programmable logic device (CPLD), 315
 with D flip-flops, 228
 digital systems, 345
 electronic design automation (EDA), 65
 with field-programmable gate array (FPGA), 315
 multiplexers, 390–401
 testing the ones counter, 400–401
 one-hot design (one flip-flop per state), 380–382
 with programmable array logic (PAL), 309, 311
 race-free, 401–403
 software race conditions, 403
 register transfer example, 352–361
 algorithmic-based behavioral description, 362
 behavioral descriptions, 361
 control logic, 360–361
 controller and datapath hardware design, 357–358
 datapath unit, 352
 HDL description of, 361–370
 register transfer representation, 358
 RTL description, 361–365
 sequence of operations, 356
 state table, 358–360
- structural description, 361, 366–370
 system chart, 353–355
 testing the design description, 365–366
 timing sequence, 355–356
 at register transfer level (RTL), 161, 334–414
 synchronous sequential logic, 161
 top-down, 161
 Design entry, 107
 Design procedure, synchronous sequential logic, 225–234
 Digital age, 1
 Digital computers, 1–3
 general-purpose, 2
 Digital integrated circuits, 471–510
 bipolar transistors:
 base-emitter graphical characteristic, 479
 characteristics of, 477–481
 collector and base currents, 478
 dc current gain, 479
 graphical collector-emitter characteristics, 479
 pulled down output, 479
 pulled out output, 479
 saturation region, 479
 types of, 477
 CMOS transmission gate circuits, 501–504
 basic circuit of, 501
 bilateral switch, 501–502
 connection to inverter, 501–502
 exclusive-OR gate, construction of, 502–503
 gated D latch, construction of, 503–504
 master-slave D flip-flop, construction of, 504–505
 multiplexer construction, 503
 complementary MOS (CMOS) circuits, 498–501
 characteristics of, 500–501
 CMOS digital logic family, 501
 CMOS transmission gate circuits, 501–504
 examples of, 498–500
 fabrication process, 501
 graphic symbols, 500
 inverter, 498
 two-input NOR gate, 500
 diodes, 479–480
 DTL digital logic family:
 analysis of, 482–483
 fan-out, 483

- NAND gate, 482
 power dissipation of a DTL gate, 483
 emitter-coupled logic (ECL), 493–495
 basic circuit, 493
 defined, 493
 external wired connection of two OR outputs, 495
 graphic symbol, 495
 internal temperature- and voltage-compensated bias circuit, 493
 internal wired connection of two OR outputs, 495
 propagation delay, 494–495
 metal-oxide semiconductor (MOS), 495–498
 advantage of, 497
 basic structure of, 495
 channel, 495
 depletion mode, 496
 diffused channel, 496
 drain, 495
 enhancement mode, 496
 gate, 495
 graphic symbols, 496
n-channel MOS, 496–497
p-channel MOS, 496–497
 source, 495–496
 types of, 496
 RTL digital logic family:
 analysis of, 481
 fan-out, 481–482
 NOR gate, 481
 switch-level modeling, 505–508
 transmission gate, 506–507
 transistor-transistor logic, 484–493
 advanced low-power Schottky TTL gate, 485
 characteristics (table), 484
 fast TTL family, 485
 high-speed TTL gate, 484–485
 low-power Schottky TTL, 485
 low-power TTL gate, 484
 open-collector output gate, 485–488
 original, 484
 propagation delay, 484
 Schottky TTL gate, 484–485, 489–491
 standard, 484
 three-state gate, 491–493
 totem-pole output, 488–489
 Digital logic circuits, 27–28
 Digital logic gates, 57–62
 exclusive-OR gate, 59
 extension to multiple inputs, 59–61
 integrated circuits, 63–65
 computer-aided design, 64–65
 digital logic families, 63–64
 levels of integration, 63
 laboratory experiment, 519–520
 NAND circuit, 520
 propagation delay, 519–520
 truth tables, 519
 universal NAND gate, 520
 waveforms, 519
 NAND function, 59
 positive and negative logic, 61
 Digital logic trainers, 511–512
 Digital systems, 1–3
 defined, 2, 334
 logic design of, 345
 relationship between control logic and data-processing operations in, 345–346
 Digital versatile disk (DVD), 2
 Diminished radix, 10
 Diminished radix complement, 10
 Diodes, 479–480
 symbol and characteristic, 480
 Direct (dedicated) interconnect lines, 317
 Direct inputs, flip-flops, 194–195
 Direct reset input, flip-flops, 194
 Distributed RAM, 317
 Distributive law, 37
 Divide-by-*N* counter, 265
 Don't-care conditions, 86–88
 DRAM, See Dynamic RAM (DRAM)
 DTL digital logic family:
 analysis of, 482–483
 fan-out, 483
 NAND gate, 482
 power dissipation of a DTL gate, 483
 DTL (diode–transistor logic), 471
 Duality, 41
 Dual-trace oscilloscope, 512
 Dynamic hazard, 453
 Dynamic memory, refreshing, 291
 Dynamic RAM (DRAM), 291
 address coding of, 295
E
 ECL (emitter-coupled logic), 471
 Edge-sensitive cyclic behavior, 344
 Edge-triggered *D* flip-flop, 189–191, 531
 graphic symbol for, 191
 hold time, 191
 master, 189–190
 setup time, 191
 slave, 189–190
 with three *SR* latches, 190–191
 with two *D* latches and an inverter, 189–190
 Electrically erasable PROM (EEPROM/E²PROM), 304
 Electronic design automation (EDA), 65
 Emitter-coupled logic (ECL), 493–495
 basic circuit, 493
 defined, 493
 external wired connection of two OR outputs, 495
 graphic symbol, 495
 internal temperature- and voltage-compensated bias circuit, 493
 internal wired connection of two OR outputs, 495
 propagation delay, 494–495
Enable input, 288
 Encoders, 150–152
 octal-to-binary, truth table for, 150
 priority, 151–152
 endmodule (keyword), 109
 Erasable PROM (EPROM), 304
 Error detection scheme, parity bit as, 296
 Error detection/correction, 296–299
 Hamming code, 296–298, 299
 single-error correction, double-error detection, 298–299
 Error-correcting code, 296
 Error-detecting code, 25
 Essential hazards, 456–457
 Event control operator, 208
 Excess-3 code, 21–22
 Excitation equations, flip-flops, 200
 Excitation table, 229
 Exclusive-NOR function (XNOR), 57
 Exclusive-OR gate, 59
 Exclusive-OR symbol (\oplus), 55
 Exclusive-OR (XOR) function, 57, 101–102, 104
F
 Fan-in, 64
 Fan-out, 64, 473–474
 Fast TTL family, 485
 Fault simulation, 108
 Feedback shift register, 537
 Feedback-free continuous assignment, 403
 Field, 37–38
 Field-effect transistor (FET), 473, 495
 Field-programmable gate array (FPGA), 65, 284, 311, 315, 343
 design with, 315
 logic block, 315
 Xilinx FPGAs, 316
 Xilinx Spartan II FPGAs, 323–327
 Xilinx Spartan XL FPGAs, 322–323
 Xilinx Virtex FPGAs, 327–329

- Field-programmable logic sequencer (FPLS), 313
- Finite state machines, Mealy and Moore models of, 206–207
- First-in, first-out register files (FIFOs), 320–321
- Five-variable map, 81–83
- Flash memory devices, 304
- Flip-flops, 183–184, 188–195, 242
characteristic equations, 194
characteristic tables, 193–194
construction of, 188–189
defined, 183
direct inputs, 194–195
dynamic indicator, 191
edge-triggered *D* flip-flop, 189–191
input equations, 199–200
JK flip-flops, 192
laboratory experiment, 530–532
 D latch, 530
 edge-triggered flip-flop, 531
 IC flip-flops, 531–532
 master-slave flip-flop, 530
 SR latch, 530
operation of, 189
operations performed with, 192
as registers, 335
and signal transition, 189
symbols, 568–570
T flip-flops, 192
timing of the response of, 191
- Flow table, 420–422
defined, 420
examples of, 420
obtaining the logic diagram from, 422
primitive, 421
- Flowcharts, 346
- for loop, 340–341
- forever loop, 340–341
- Four-bit data-storage register, 244
- Four-to-one-line multiplexers, 153
- Four-variable map, 76–80
 prime implicants, 79–80
- FPGA (field-programmable gate array), 284
- Full adder, 130, 131–133, 527
- Function blocks, 315
- G**
- Gate array, 315
- Gate instance, 110
- Gate instantiation, 110
- Gate-level minimization, 70–121
 AND–OR–INVERT function, 96
 implementation, 97–99
- defined, 70
- don't-care conditions, 86–88
- exclusive-OR (XOR) function, 101–102
- five-variable map, 81–83
- four-variable map, 76–80
 prime implicants, 79–80
- gate delays, 110–113
- hardware description language (HDL), 106–116
- Karnaugh map (K-map), 70–71
- map method, 70–71
- multilevel NAND circuits, 92–93
- NAND gate, 89–90
- nondegenerate forms, 97
- NOR gate, 93–96
- odd function, 102–104
- OR–AND–INVERT function, 96
 implementation, 98–100
- parity checker, 104–106
- parity generation, 104–106
- product-of-sums simplification, 83–86
- three-variable map, 72–76
- two-level implementation, 90–92
- two-variable map, 71–72
- Gate-level (structural) modeling, 159
- Giga (G), 4
- Gray code, 22–23
- H**
- Half adder, 130–131, 527
- Hamming code, 296–298
 modified, 299
 using for data words, 298
- Hardware algorithm, 346
- Hardware description language (HDL), 65, 106–116, 159, 315
 Boolean expressions, 113–114
 defined, 106
 design entry, 107
 as documentation language, 107
 fault simulation, 108
 logic simulation, 107
 module declaration, 108–109
 register transfer level (RTL) in, 336–345
 for registers and counters, 269–276
 switch-level modeling, 505–508
 transmission gate, 506–507
 test bench, 107
 timing verification, 107–108
 user-defined primitives, 114–116
- Hardware signal generators, 112
- Hazards, 452–457
 in combinational circuits, 452–454
 defined, 452
- detection of, 453
- dynamic, 453
- essential, 456–457
- implementation with SR latches, 454–456
- remedy for eliminating, 454
- in sequential circuits, 454
- static 0-hazard, 453
- static 1-hazard, 453
- Hexadecimal (base-16) number system, 3–4
- Hexadecimal numbers, 8–9
- High impedance, 159
- High-impedance state, 156
- High-speed TTL gate, 484–485
- Huntington, E. V., 38
- I**
- IC digital logic families, 471
 basic circuits in, 471
 bipolar junction transistor (BJT), 473
 data book, 471–472
 field-effect transistor (FET), 473
 NAND gates, 471–472
 NOR gates, 471–472
 special characteristics, 473–477
 fan-out, 473–474
 noise margin, 476–477
 power dissipation, 474–475
 propagation delay, 475–476
- Identity element, 37
- Implication table, 440–441
- Incompletely specified functions, 87
- Information transfer, between registers, 335
- initial** block, 218
- Input equations, flip-flops, 199–200
- Instantiation, 110, 160
- Institute of Electronics and Electrical Engineers (IEEE), 65
- integer** data type, 342
- Integrated circuit RAM units, 291
- Integrated circuits (ICs), 63–65, 471
 computer-aided design, 64–65
 digital logic families, 63–64
 levels of integration, 63
- Interconnect resources, 317–318
 programmable, 319
- Intra-assignment delay, 274
- Inverse, 37
- J**
- JK* flip-flops, 192
 analysis of clocked sequential circuits with, 204–206

analysis with, 201–204
 characteristic table, 193
 Johnson counters, 268–269
 Junction field-effect transistor (JFET), 495

K

Karnaugh map (K-map), 70–71, 343
 Keywords, 108–109
 Kilo (k), 4

L

Laboratory experiments, 511–558
 adders and subtractors
 (experiment 7), 527
 adder-subtractor (four-bit), 528–529
 full adder, 527
 half adder, 527
 magnitude comparator, 529–530
 parallel adder, 528
 asynchronous sequential circuits
 (experiment 18), 553
 binary and decimal numbers
 (experiment 1), 516
 BCD count, 517–518
 binary count, 516–517
 counts, 518
 oscilloscope display, 517
 output pattern, 517–518
 binary multiplier (experiment 17),
 549–553
 block diagram, 549–550
 checking, 552–553
 control of registers, 550–552
 datapath design, 552
 design of control circuit, 552
 multiplication example, 552
 Boolean function simplification
 (experiment 3), 520–522
 Boolean functions in sum-of-minterms form, 522
 complement, 522
 gate ICs, 521
 logic diagram, 521–522
 clock-pulse generator (experiment 15),
 545–547
 circuit operation, 545–546
 clock-pulse generator operation,
 546–547
 IC timer, 545
 code converters (experiment 5),
 524–526
 Gray code to equivalent binary, 524
 nine's complements, 525
 seven-segment display, 525–526

combinational circuits (experiment 4),
 522–524
 decoder and truth table block
 diagram, 523–524
 decoder implementation, 523–524
 design example, 523
 majority logic, 523
 parity generator, 523
 counters (experiment 10), 533–535
 binary counter with parallel load,
 534–535
 decimal counter, 534
 ripple counter, 534
 synchronous counter, 534
 digital logic gates (experiment 2),
 519–520
 NAND circuit, 520
 propagation delay, 519–520
 truth tables, 519
 universal NAND gate, 520
 waveforms, 519
 digital logic trainers, 511–512
 dual-trace oscilloscope, 512
 flip-flops (experiment 8), 530–532
 D latch, 530
 edge-triggered flip-flop, 531
 IC flip-flops, 531–532
 master-slave flip-flop, 530
 SR latch, 530
 gate ICs needed for, 512
 graphic symbols, 515
 IC type 7493 ripple counter, 512
 operation of, 512–515
 integrated circuits required, 515
 lamp handball (experiment 15), 541–545
 circuit analysis, 544
 counting the number of losses, 544
 IC type 74194, 542
 Lamp Ping-Pong™, 545
 logic diagram, 542–544
 playing the game, 544
 logic breadboard suitable for
 performing, 511
 medium-scale integration (MSI)
 circuits, 512
 memory unit (experiment 14), 539–541
 IC RAM, 539–540
 memory expansion, 541
 ROM simulator, 541
 testing the RAM, 540–541
 multiplexer design (experiment 6),
 526–527
 specifications, 527
 parallel adder and accumulator
 (experiment 16), 547–549
 block diagram, 547
 carry circuit, 548
 checking the circuit, 548
 circuit operation, 549
 control of register, 547
 detailed diagram of circuit, 548
 sequential circuits (experiment 9),
 532–533
 counter design, 533
 state diagram, 533
 up-down counter with enable, 533
 serial addition (experiment 12),
 538–539
 serial adder, 539
 serial adder-subtractor, 539
 testing the adder, 539
 shift registers (experiment 11), 535–538
 bidirectional shift register, 537
 bidirectional shift register with
 parallel load, 537–538
 feedback shift register, 537
 IC shift register, 535–536
 ring counter, 537
 small-scale integration (SSI)
 circuits, 512
 Verilog HDL simulation experiments
 and rapid prototyping with
 FPGAs, 553
 experiment 1, 554
 experiment 2, 554–555
 experiment 4, 555–556
 experiment 5, 556
 experiment 7, 556
 experiment 8, 556
 experiment 9, 557
 experiment 10, 557
 experiment 11, 557
 experiment 13, 557–558
 experiment 14, 558
 experiment 16, 558
 experiment 17, 558
 Lamp handball (laboratory experiment),
 541–545
 circuit analysis, 544
 counting the number of losses, 544
 IC type 74194, 542
 Lamp Ping-Pong™, 545
 logic diagram, 542–544
 playing the game, 544
 Large-scale integration (LSI) devices, 63
 Latches, 184–188
 D latch (transparent latch), 187–188
 reset state, 185
 sensitivity of, 184
 set state, 185

- Latches (*cont.*)
SR latch, 185–187
 trigger, 188
- Latch-free design, 403–404
- Literals, 46
- Load operation, registers, 244, 334
- Logic circuits, *See* Digital systems
- Logic diagram:
 obtaining output Boolean functions from, 124
 of three-bit binary counter, 234
- Logic gates, 30–31
- Logic operations, digital systems, 336
- Logic operators, Verilog 2001 HDL, 339
- Logic operators, for binary words, 338
- Logic simulation, 107
- Logic simulators, 122
- Logic synthesis, 343–345
 advantages to designer, 345
assign statement, 343
 tools, 343
- Logical operators, Verilog 2001 HDL, 339
- Loop statements, 340–341
- Low-power Schottky TTL, 485
- Low-power TTL gate, 484
- M**
- Magnetic disk, 290–291
- Magnitude comparator, 143–145, 529–530
 four-bit, 145
- Mask programming, 303
- Master-slave flip-flop, 530
- Maximal compatibles, 444–445
- Mealy FSM (Mealy machine), 206
- Mealy model, 206–207
- Mealy_Zero_Detector*, 215–216
- Medium-scale integration (MSI)
 circuits, 512
- Medium-scale integration (MSI)
 devices, 63
- Mega (M), 4
- Mem*, 288
- Memory:
 access time, 289
 address, 286
 architecture of, 285
 communication between the environment and, 285
 cycle time, 289
 integrated circuit RAM units, 291
 programmable logic device (PLD), 284
 random-access (RAM), 284
 sequential-access, 290
 types of, 290–291
- Memory cell, 291–292
- Memory chip, control inputs to, 288
- Memory cycle timing waveforms, 289–290
- Memory decoding, 291–295
 address multiplexing, 294–295
 coincident decoding, 293–294
 internal construction, 291–292
- Memory depth, 288
- Memory description in HDL, 288–289
- Memory enable, 287, 289
- Memory system, mode of access of, 290
- Memory timing, 289
- Memory units, 284–287
 block diagram, 285–286
 capacity of, 285
 defined, 284–285
 laboratory experiment, 539–541
 IC RAM, 539–540
 memory expansion, 541
 ROM simulator, 541
 testing the RAM, 540–541
- operation of, 288
- reliability of, 296
- volatile, 291
- words, 285, 287
- memword*, 288
- Merger diagram, 444
- Metal-oxide semiconductor (MOS):
 advantage of, 497
 basic structure of, 495
 channel, 495
 depletion mode, 496
 diffused channel, 496
 drain, 495
 enhancement mode, 496
 gate, 495
 graphic symbols, 496
n-channel MOS, 496–497
p-channel MOS, 496–497
 source, 495–496
 types of, 496
- Metal-oxide-semiconductor field-effect transistor (MOSFET), 473
- Module, 207
- module ... endmodule** (keyword pair), 109
- Module declaration, 108–110
- Modules, 108–110, 217
- Modulo-*N* counter, 265
- Moore FSM (Moore machine), 206
- Moore model, 206–207
- MOS, *See* Metal-oxide semiconductor (MOS)
- Multilevel NAND circuits, 92–93
- Multiple-row method, 450–452
- Multiplexers, 152–158, 313
 Boolean function implementation, 154–156
 data selector, 154
 defined, 152
 design example, 393–400
 testing the ones counter, 400–401
- design with, 390–401
 laboratory experiment, 526–527
- four-to-one-line, 153
- graphics symbols for, 567
- implementing a Boolean function with, 156
- implementing a four-input function with, 157
- input conditions, 393
- quadruple two-to-one-line, 155
- three-state gates, 156–158
- two-to-one-line, 152–153, 153
- N**
- NAND gate, 89–90
- n*-bit binary code, 17–18
- Negation (–) operator, 338
- negedge** (keyword), 209
- Nets, 164
- Noise, defined, 476
- Noise margin, 64, 476–477
- Nonblocking assignments, 209–210, 337–338
- Noncritical race, 422
- Nondegenerate forms, 97
- Nonvolatile memory, 291
- NOR gate, 93–96
- NOT operation, 29
- npn* type, bipolar transistor, 477–478
 silicon transistor parameters, 479
- n*-to-*m*-line decoders, 146
- Number-base conversions, 5–7
- O**
- Octal number system, 4
- Octal numbers, conversion to hexadecimal, 9
- Octal-to-binary encoder, truth table for, 150
- Odd function, 102–104
- One-hot assignment, 224–225
- One-hot design, 380–382
- Open Verilog International (OVI), 108
- Open-collector output gate, 485–488
 AND–OR–INVERT function, 487
 applications, 486
 forming a common bus line, 487–488
- NAND gate, 485
- wired-AND, 487

- Operator precedence, 43–44
OR gate, conventional and array logic diagrams for, 285
OR operation, 29
 Output equations, flip-flops, 200
 Overflow, 138–139
- P**
- PAL**, *See* Programmable array logic (PAL)
 Parallel adder, 528
 laboratory experiment, 547–549
 block diagram, 547
 carry circuit, 548
 checking the circuit, 548
 circuit operation, 549
 control of register, 547
 detailed diagram of circuit, 548
 Parallel load:
 bidirectional shift register with, 537–538
 binary counters with, 534–535
Clear input, 262–264
CLK input, 264
Count input, 264
Load input, 264
 registers with, 244–245
 Parallel multiplier, behavioral description of, 388–390
 Parallel-load control, shift registers, 251
parameter (keyword), 213
 Parity bit, 25
 as error detection scheme, 296
 Parity checker, 104–106
 Parity generation, 104–106
 Parity generator, combinational circuits, 523
 PIP-based interconnection, architecture of, 319–320
PLA, *See* Programmable logic array (PLA)
PLD, *See* Programmable logic device (PLD)
pnp type, bipolar transistor, 477–478
posedge (keyword), 209
 Positive-edge-triggered *D* flip-flop, 194–195
 Power dissipation, 64, 474–475
 Powers of two (table), 5
 Predefined primitives, 110
 Preset inputs, flip-flops, 194–195
 Prime implicants, 79–80
 Primitive flow table, 421, 457–458
 Primitive gates, 110
 Primitives, 110
- Priority encoders, 151–152
 four-input, 152
 maps for, 151
 truth table for, 151
 Procedural assignments, 337
 Product of sums, 54
 expression, 95
 simplification, 83–86
Programmable array logic (PAL), 284–285, 309–311
 commercial, 309
 defined, 309
 designing with, 309, 311
 fuse map for, 311
 programming table, 309–311
Programmable logic array (PLA), 284, 305–308
 defined, 305
 designing a digital system with, 307
 fuse map of, 306, 308
 implementing a combinational circuit with, 307–308
 internal logic of, 305
 programming table:
 generation of, 308
 sections of, 306
 size of, 307
Programmable logic device (PLD), 65, 284–285, 343
 design with, 315
Programmable read-only memory (PROM), 303–304
Programming, 284–285
 Propagation delay, 64, 475–476
 digital logic gates (laboratory experiment), 519–520
 emitter-coupled logic (ECL), 494–495
 IC digital logic families, 475–476
 transistor-transistor logic (TTL), 484
- Q**
- Quadruple two-to-one-line multiplexers, 155
 Qualifying symbols, 562–564
 Qualitative analysis, 480
 Quantitative analysis, 480
- R**
- Race conditions, 422–424
 critical race, 422–423
 avoiding, 447
 examples of, 423
 cycles, 423–424
 noncritical race, 422
- Race-free design, 401–403
 software race conditions, 403
 Race-free state assignment, 446–452
 four-row flow-table example, 449–450
 multiple-row method, 450–452
 three-row flow-table example, 447–449
 Radix, 3–4, 10–11
 Radix complement, 10–11
RAM, *See* Random-access memory (RAM)
 Random-access memory (RAM), 284–291
 commercial, word capacity of, 292
 memory description in HDL, 288–289
 memory, types of, 290–291
 symbol for, 574
 timing waveforms, 289–290
 write and read operations, 287–288
 Read cycle, 289
Read input, 285
Read operation, 284
Read-only memory (ROM), 284, 299–305
 block diagram, 299–300
 combinational circuit
 implementation, 302
 combinational programmable logic device (PLD), 304–305
 defined, 299
 electrically erasable PROM (EEPROM/E²PROM), 304
 erasable PROM (EPROM), 304
 flash memories, 304
 internal binary storage of, 300
 internal operation of, 302
 mask programming, 303
 number of words in, 299
 programmable read-only memory (PROM), 303–304
 programming, 300–301
 truth table, 301
 types of, 303–304
ReadWrite input, 288
Read/write signals, 289
 Rectangular-shape symbols, 559–561
 Reduction operators, 338
reg variable, 342
 Register operations, 334
 Register symbols, 570–572
 Register transfer, 26–28
 Register transfer level (RTL), 2
 algorithmic state machines (ASMs), 345–352
 design example, 352–361
 binary multiplier:
 control state diagram for, 376
 HDL description of, 382–389

- Register transfer level (RTL) (*cont.*)
 continuous assignments, 337
 control logic, 376–382
 design at, 334–414
 digital system represented at, 334
 in HDL, 336–345
 HDL operators, 338–340
 logic synthesis, 343–345
 loop statements, 340–341
 latch-free design, 403–404
 multiplexers, design with, 390–401
 notation, 334–335
 procedural assignments, 337–338
 race-free design, 401–403
 sequential binary multiplier, 370–376
- Register transfer operations, 334, 336
- Registers, 26, 242–253, 334, *See also*
 Register transfer level (RTL)
 defined, 242, 335
 four-bit data-storage register, 244
 HDL for, 269–276
 ripple counter, 274–276
 shift register, 269–273
 synchronous counter, 273–274
 loading, 244
 with parallel load, 244–245
 shift registers, 245–253
 defined, 245
 serial addition, 248–250
 serial input, 246
 serial output, 246
 serial transfer, 246–248
 simple, 245–246
 universal, 250–253
 types of, 242–243
 updating, 244
- Relational operators, Verilog 2001
 HDL, 339
- repeat loop, 340
- Reset state, latches, 185
- Ring counters, 267–268, 537
- Ripple counters, 253–258, 534
 BCD, 256–258
 binary, 253–256
 defined, 253, 256
 HDL for, 274–276
- ROM (read-only memory),
See Read-only memory (ROM)
- RTL digital logic family:
 analysis of, 481
 fan-out, 481–482
 NOR gate, 481
- RTL (resistor-transistor logic), 471
- S
- Schematic capture, 65
- Schematic entry, 65
- Schottky transistor, defined, 489
- Schottky TTL gate, 484–485, 489–491
 symbol for Schottky
 transistors/diodes, 490
- Scratchpad memories, 321
- Sensitivity list, 208
- Sequence detector:
 maps for, 228
 state diagram for, 227
 state table for, 228
- Sequential binary multiplier, 370–376
 ASMD chart, 373–376
 register configuration, 372–373
- Sequential circuits, 182–184, 415–470
 asynchronous, 183
 block diagram, 182
 hazards in, 454
 laboratory experiment, 532–533
 counter design, 533
 state diagram, 533
 up-down counter with enable, 533
 synchronous, 183
- Sequential (or simple) programmable logic device (SPLD), 311, 313
- Sequential programmable devices, 311–329
- complex programmable logic device (CPLD), 311, 313–315
 design with, 315
- configurable logic block (CLB), 317
- distributed RAM, 317
- enhancements, 320–321
- field-programmable gate array (FPGA), 65, 284, 311, 315
 design with, 315
 logic block, 315
- Xilinx FPGAs, 316
- Xilinx Spartan II FPGAs, 323–327
- Xilinx Spartan XL FPGAs, 322–323
- Xilinx Virtex FPGAs, 327–329
- interconnect resources, 317–318
- I/O block (IOB), 320
- sequential (or simple) programmable logic device (SPLD), 311, 313
- Xilinx:
 basic architecture, 316–317
 FPGAs, 316
- Sequential-access memory, 290
- Serial adder, 248, 539
 second form of, 250
 state table for, 250
- Serial addition, 248–250
 laboratory experiment, 538–539
 serial adder, 539
 serial adder-subtractor, 539
 testing the adder, 539
- Serial bit stream, 227
- Serial input, 246
- Serial output, 246
- Serial transfer, 246–248
- Set, 36
- Set state, latches, 185
- Shannon, C. E., 38
- Shared-row method, 451
- Shift operation, registers, 334
- Shift operations, digital systems, 336
- Shift operators, Verilog 2001 HDL, 339
- Shift register, HDL for, 269–273
- Shift registers, 245–253, 321
 bidirectional, 251
 clear control, 251
 clock input, 251
 defined, 245
 laboratory experiment, 535–538
 bidirectional shift register, 537–538
 bidirectional shift register with
 parallel load, 537–538
 feedback shift register, 537
 IC shift register, 535–536
 ring counter, 537
- parallel-load control, 251
- serial addition, 248–250
- serial input, 246
- serial output, 246
- serial transfer, 246–248
- shift-left control, 251
- shift-right control, 251
- simple, 245–246
- unidirectional, 251
- universal, 250–253
- Shift-left control, shift registers, 251
- Shift-right control, shift registers, 251
- Signed binary numbers, 14–17
 arithmetic addition, 16
 arithmetic subtraction, 17
- Signed-complement system, 14
- Signed-magnitude convention, 14
- Simple shift registers, 245–246
- Simple_Circuit_prop_delay*, 111–112
- Single-error correction, double-error detection, 298–299
- Single-pass behavior, 207
- Small-scale integration (SSI) circuits, 512
- Small-scale integration (SSI) devices, 63
- Software race conditions, 403
- Spartan chips, 320–321
- Spartan device families, comparison chart, 324
- Spartan devices, 317
- Spartan II FPGAs, 323–327
 device attributes (table), 324
- Spartan XL FPGAs, 322–323
 architecture of, 323
 device attributes (table), 323

- SPLD. *See* Sequential (or simple) programmable logic device (SPLD)
- SR* latch, 185–187
- SRAM. *See* Static RAM (SRAM)
- Stable circuits, 424–425
- Standard forms:
- Boolean algebra, 48–55
 - defined, 54
 - expression of a Boolean function in, 55
 - product of sums, 54
 - sum of products, 54–55
- Standard graphic symbols, 559–576
- combinational element symbols, 566–568
 - counter symbols, 572–574
 - dependency notation, 564–566
 - flip-flop symbols, 568–570
 - qualifying symbols, 562–564
 - RAM symbol, 574
 - rectangular-shape symbols, 559–561
 - register symbols, 570–572
- State assignment, 224–225
- State diagram, 199, 213–217
- compared to a state table, 198
 - reducing, 223–224
 - for sequence detector, 227
- State equations, 196–197
- Boolean expressions for, 197
 - defined, 196–197
- State machine, defined, 346
- State reduction, 220–223
- State table, 197–198
- binary form of, 225
 - compared to a state diagram, 198
 - and JK flip-flop inputs, 231
 - reducing, 222–223
 - sections, 198
 - for sequence detector, 228
 - for three-bit binary counter, 231–233
- State tables, reduction of, 439–441
- Static 0-hazard, 453
- Static 1-hazard, 453
- Static RAM (SRAM), 291
- Storage elements:
- defined, 184
 - flip-flops, 188–195
 - latches, 184–188
- Sum of products, 54–55
- Switch-level modeling, 505–508
- transmission gate, 506–507
- Switch matrices, and CLB architecture, 317–319
- Switching algebra, 38
- Synchronous counters, 258–264, 534
- BCD counter, 260–262
 - state table for, 260–262
- binary counter, 258–260
- four-bit, 259
- binary counter with parallel load, 262–265
- Clear* input, 262–264
 - CLK* input, 264
 - Count* input, 264
 - Load* input, 264
- defined, 253
- HDL for, 273–274
- up-down binary counter, 260
- four-bit, 261
- Synchronous RAM (SelectRAM), 320–321
- Synchronous sequential circuits, 183, 225
- Synchronous sequential logic, 182–241
- clocked sequential circuits, analysis of, 195–207
 - design procedure, 225–234
 - sequential circuits, 182–184
 - state assignment, 224–225
 - state reduction, 220–223
 - storage elements:
 - defined, 184
 - flip-flops, 188–195
 - latches, 184–188 - synthesizable HDL models of sequential circuits, 207–220
- Syndrome, 296
- Synthesis, 226
- Synthesis tools, 315
- Synthesizable HDL models of sequential circuits, 207–220
- behavioral modeling, 207–210
 - clocked sequential circuits, structural description of, 217–220
 - flip-flops and latches, 210–213
 - state diagram, 199
- System primitives, 114
- T**
- T* flip-flops, 192
- analysis of clocked sequential circuits with, 204–206
 - analysis with, 204–206
 - characteristic table, 193–194
 - conditions, 194
- t_Simple_Circuit_prop_delay*, 112
- Tape unit, 290
- Tera (T), 4
- Test access port (TAP) controller, 320
- Test bench, 107, 111
- Test bench module, 218
- Three-bit binary counter:
- logic diagram of, 234
 - maps for, 234
 - state diagram of, 233
 - state table for, 231–233
- Three-state buffer gate, graphic symbol for, 157
- Three-state gates, 156–158, 491–493
- buffer gate, graphic symbol of, 491–492
 - bus, creation of, 493
 - inverter, 491–492
 - output enable delay compared to output disable delay, 493
 - output states, 491
- Three-to-eight-line decoder, 146
- truth table for, 147
- Three-variable map, 72–76
- Time units, 110
- Time-delay devices, 183
- Timing verification, 107–108
- Timing waveforms, 289–290
- Top-down design, 161
- Total state, 419
- Totem-pole output, 488–489
- defined, 488
 - wired-logic connection, 489
- Transfer function, 57
- Transfer operations, digital systems, 336
- Transistors, 1
- Transistor-transistor logic (TTL):
- advanced low-power Schottky TTL gate, 485
 - characteristics (table), 484
 - defined, 471
 - fast TTL family, 485
 - high-speed TTL gate, 484–485
 - low-power Schottky TTL, 485
 - low-power TTL gate, 484
 - open-collector output gate, 485–488
 - original, 484
 - propagation delay, 484
 - Schottky TTL gate, 484–485, 489–491
 - standard, 484
 - three-state gate, 491–493
 - totem-pole output, 488–489
 - TTL gate, operation of, 471
- Transition diagram, 447
- Transition equation. *See* State equations
- Transition table, 225, 417–420, *See* State table
- of asynchronous sequential circuits, 419–420
- Transparent latch, 187–188
- Trigger, latches, 188
- Truth tables, 29
- TTL. *See* Transistor-transistor logic (TTL)
- 2421 code, 21–22
- Two-level implementation, 90–92
- Two-to-four-line decoder, with enable input, 147–148
- Two-to-one-line multiplexers, 152–153, 153

Two-valued Boolean algebra,
39–41

Two-variable map, 71–72

U

UDPs, *See User-defined primitives (UDPs)*

Unidirectional shift registers, 251

Universal NAND gate, 520

Universal shift registers, 250–253
four-bit, 252

Unknown value, 159

Unsigned binary numbers, 14

Unstable circuits, 424–425

Unused states, 224

counters with, 265–266

Updating a register, 244

User-defined primitives (UDPs), 114–116

V

Vectors, 160

Verilog HDL, 108, 159, 207, 209, 315

memory description in, 288

operators, 165, 338–340

switch-level modeling, 505–508

transmission gate, 506–507

Very large-scale integration (VLSI)

devices, 63–65

VHDL, 108, 315

Virtex FPGAs, 327–329

Volatile memory units, 291

W

Waveforms, 519

Weighted codes, 21

while loop, 340–342

Wired logic, 96

Word length, 288

Word locations, 290

Words, 285, 287

Write input, 285

Write operation, 284

X

Xilinx:

basic architecture, 316–317

FPGAs, 316

Spartan II FPGAs, 323–327

Spartan XL FPGAs, 322–323

Virtex FPGAs, 327–329

XNOR function, 57

XOR function, 57