Contents

	Preface	7
	About the author	8
1	Number System Basics	9
1.1	Decimal Numbers	9
1.2	Other Number Systems - Binary, Octal and Hexadecimal	10
1.3	Conversion between different number systems	13
1.4	Other number codes	15
2	Introduction to Logic Gates	19
2.1	AND gate	22
2.2	OR gate	25
2.3	NOT gate	27
2.4	AND implementation with OR gate and vice versa	28
2.5	NAND gate	29
2.6	NOR gate	31
2.7	Integrated circuits	32



3	Combinatorial Logic Circuits	33
3.1	Logic circuit simplification	34
3.2	Boolean algebra	35
3.3	DeMorgan's theorem	38
3.4	More examples	39
3.5	XOR and XNOR gates	43
4	Karnaugh Maps	47
4.1	Sum of products	47
4.2	Product of sums	48
4.3	K-maps	51
5	Bistable Multivibrator Circuits	67
5.1	S-R flip-flop	68
5.2	J-K flip-flop	75
5.3	D flip-flop	79
5.4	T flip-flop	82
5.5	Monostable and astable multivibrators	84



6	Arithmetic Circuits	87
6.1	Half adder	87
6.2	Full adder	89
6.3	Parallel adder	92
6.4	Parallel addition using integrated circuits	93
6.5	Parallel subtraction	94
7	Coders and Multiplexers	98
7.1	Encoder	99
7.2	Decoder	104
7.3	Multiplexer	107
7.4	De-multiplexer	111
8	Counters	114
8.1	Asynchronous up-counter	114
8.2	Asynchronous down-counter	117
8.3	Asynchronous counters with incomplete cycles	120
8.4	Synchronous counters	123

